

Asynchronous wired-logic control

- Context:
 - we've examined synchronous
 - wired logic
 - microprogrammed

Asynchronous wired-logic control


- Ideas

- asynchronous \Rightarrow
 - no clock
 - every gate (Muller model) or every feedback loop (Huffman model) has a pure, positive delay


Asynchronous \implies

- circuit must have the same behaviour *independent of all possible changes in delays*
- no critical races
- no oscillations

Huffman Model

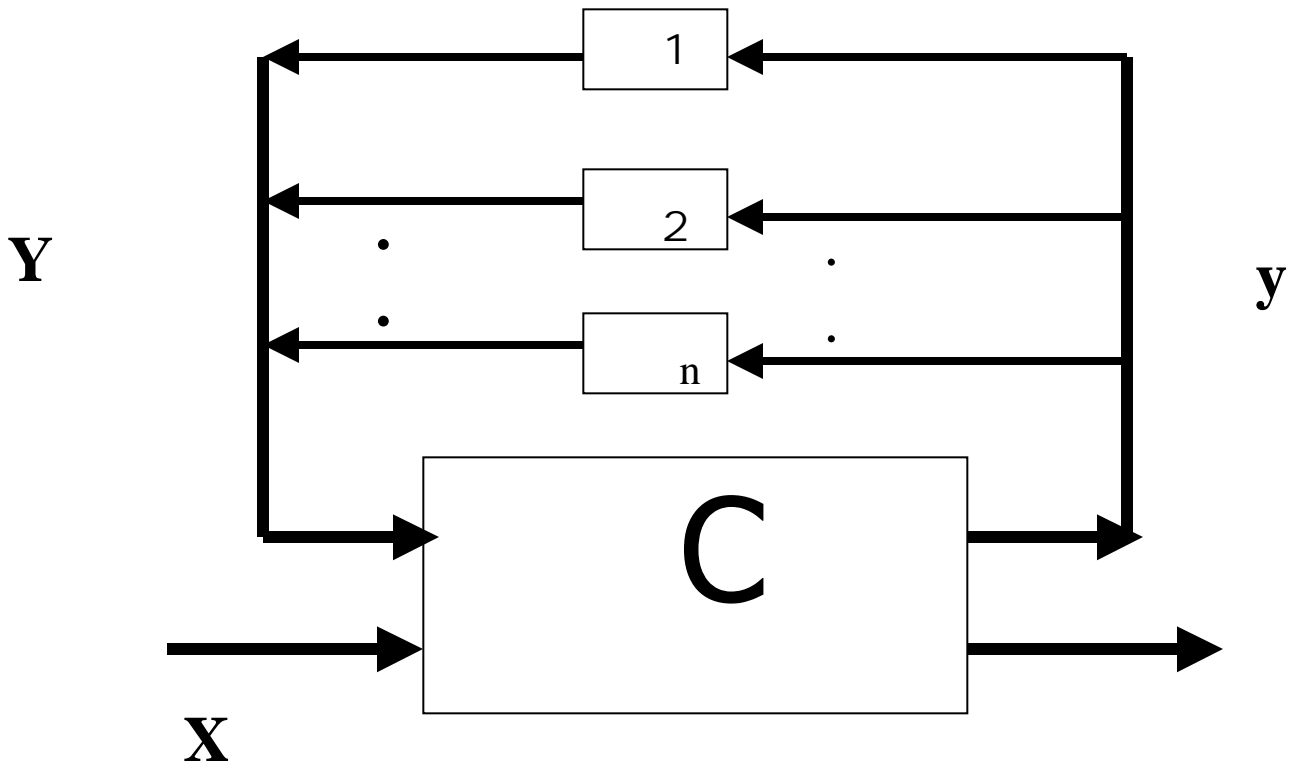


Control setup

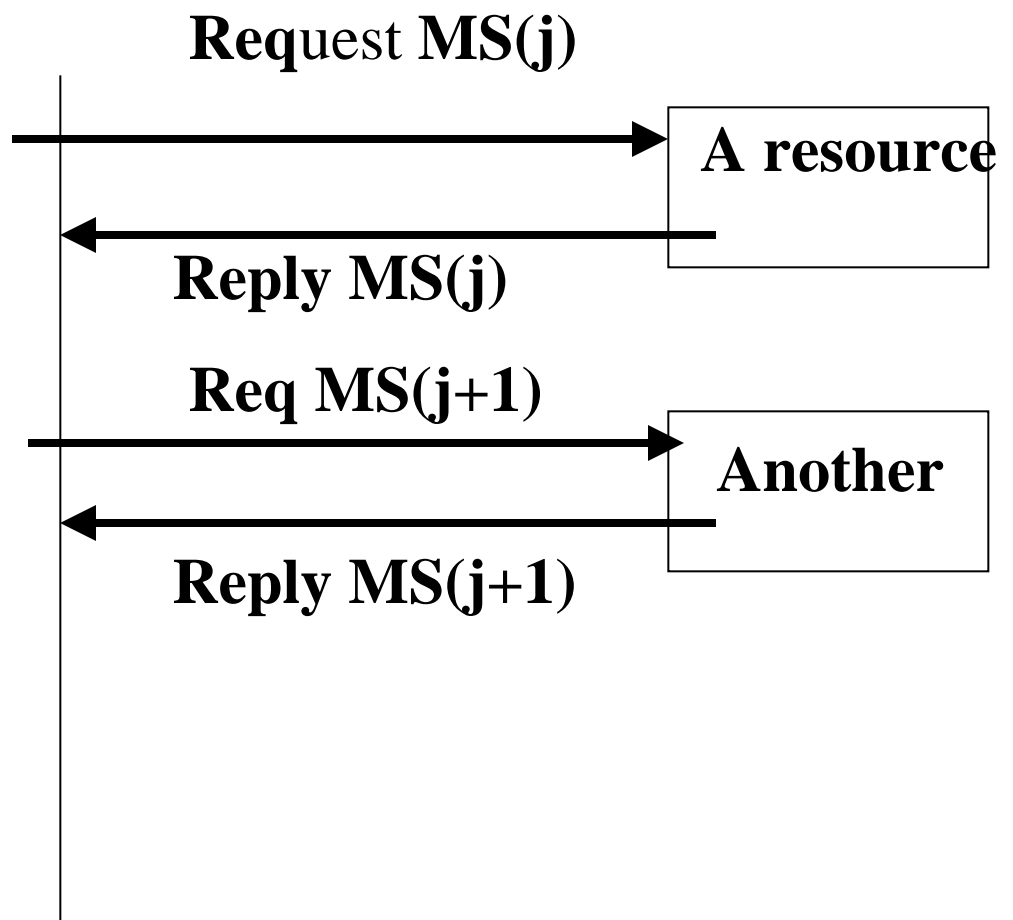

Control unit


Protocol between control & resources

 - 1] Request MS (j)
- 2] MS(j) begins
- 3] Reply “it’s done”



Protocol

 - 4] Reply heard: turn off Request
- 5] Request heard off: turn off Reply
- 6] Reply heard off: start Request MS(j+1)



NB

- Functions correctly, independent of microstep duration
- no clock
- each resource (ALU, register, bus, . . .) must generate a true reply.
- How to design the control??
 - Using 1-active SR flipflops:

